

Energy Harvesting

IEEE RFID 2026 Tutorial presented by **Greg Durgin**



Contact Info: durgin@gatech.edu

- If you would like an official-looking certificate for attendance, email me:
 - A list of each session attended
 - Session I: RF in RFID
 - Session II: Energy-Harvesting/Circuits
 - Session III: Circuits and Cryptography/Middleware
 - Session IV: Tires/PLCs, Neuromorphic RFID
 - Three things that you learned in that session

Introductions

IEEE
RFID
2026

Greg Durgin

Energy Harvesting



RFID4n: The Finest Granfalloon in All of RFID!

RFID4n crew



Degnan

Brian Degnan is a semiconductor design and process engineer with extensive experience in low power circuit design and cryptography for RFID, as well as characterizing advanced nodes at 3 nm and beyond.

Dobkin

Daniel Dobkin is the author of The RF in RFID, and has been involved in semiconductor characterization and reliability since the days when a micron was small.

Dungen

Jeffrey Dungen combines expertise in radio communications with knowledge of the software needed to exploit the capabilities of Bluetooth Low Energy and other active RF technologies.

Durgin

Gregory Durgin is a professor at the Georgia Institute of Technology, with broad experience in radio propagation, low-power circuitry, and the use of nonlinear devices in radio communications.

Sober Oversight



D'Kevin
~~Berisso~~

Kevin Berisso is the Director of the AutolD Lab at the University of Memphis, focused on the practical integration of RFID and visual code identification with automated materials handling and inventory management.

IEEE
RFID
2026

Greg Durgin

Energy Harvesting



Goals of this Talk

- Provide a Basic Understanding of How RF Energy-Harvesting works
- Provide some history into the development of RFID RF harvesting technology
- Learn circuits the FUN way! (graphically)
- Develop a feel for the performance, limitations, and future of passive RFID technologies
a.k.a. Why does RFID work the way it works?



Outline of this Tutorial

- Introduction
- Basics of Wireless Power Transfer
- What Comes Out of an Antenna?
- Converting RF to DC
- Conversion Efficiency
- Now Let's do it in CMOS
- The Future



Basics of Wireless Power Transfer


IEEE
RFID
2026

Greg Durgin

Energy Harvesting




Taxonomy of Wireless Power Transfer

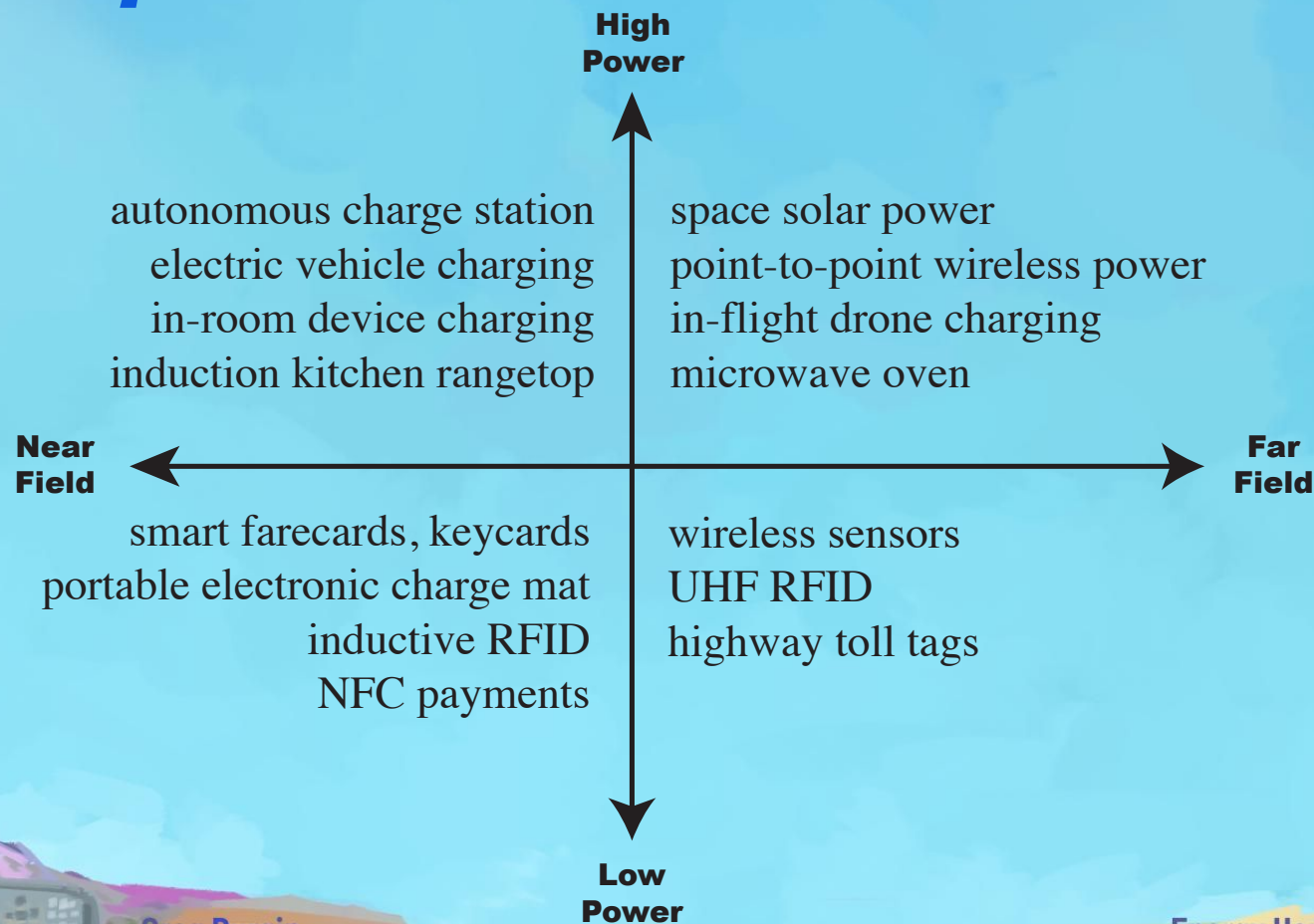


Basic Parts of All Wireless Power Systems

Block Diagram of a Wireless Power System

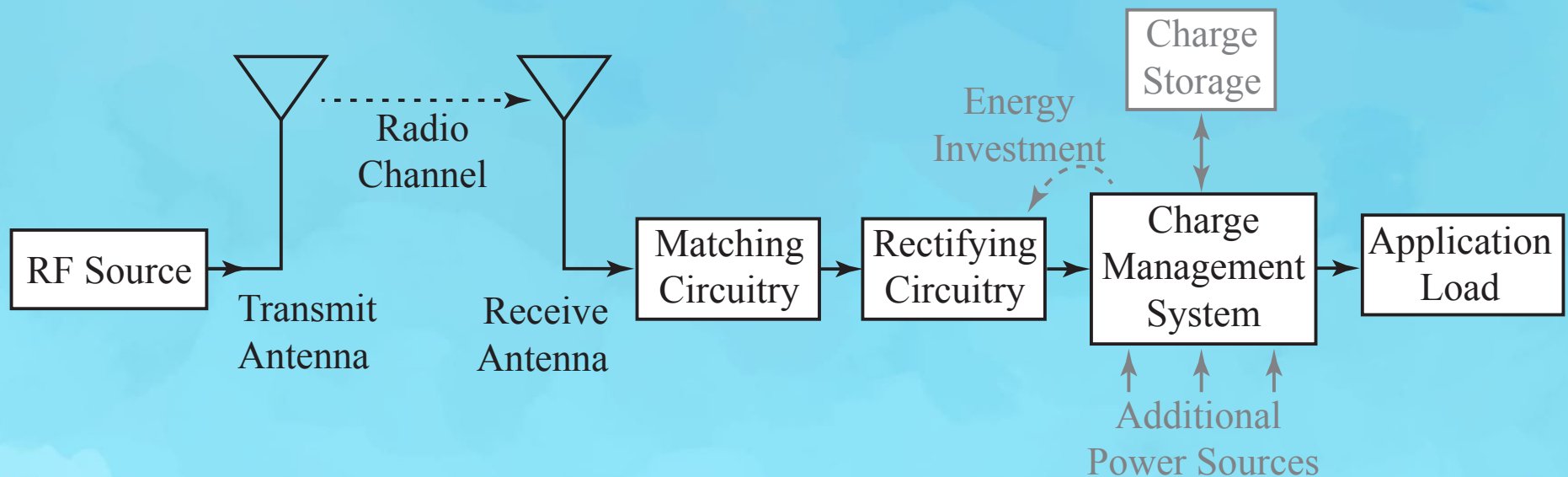

Basic Components of an RFID Tag

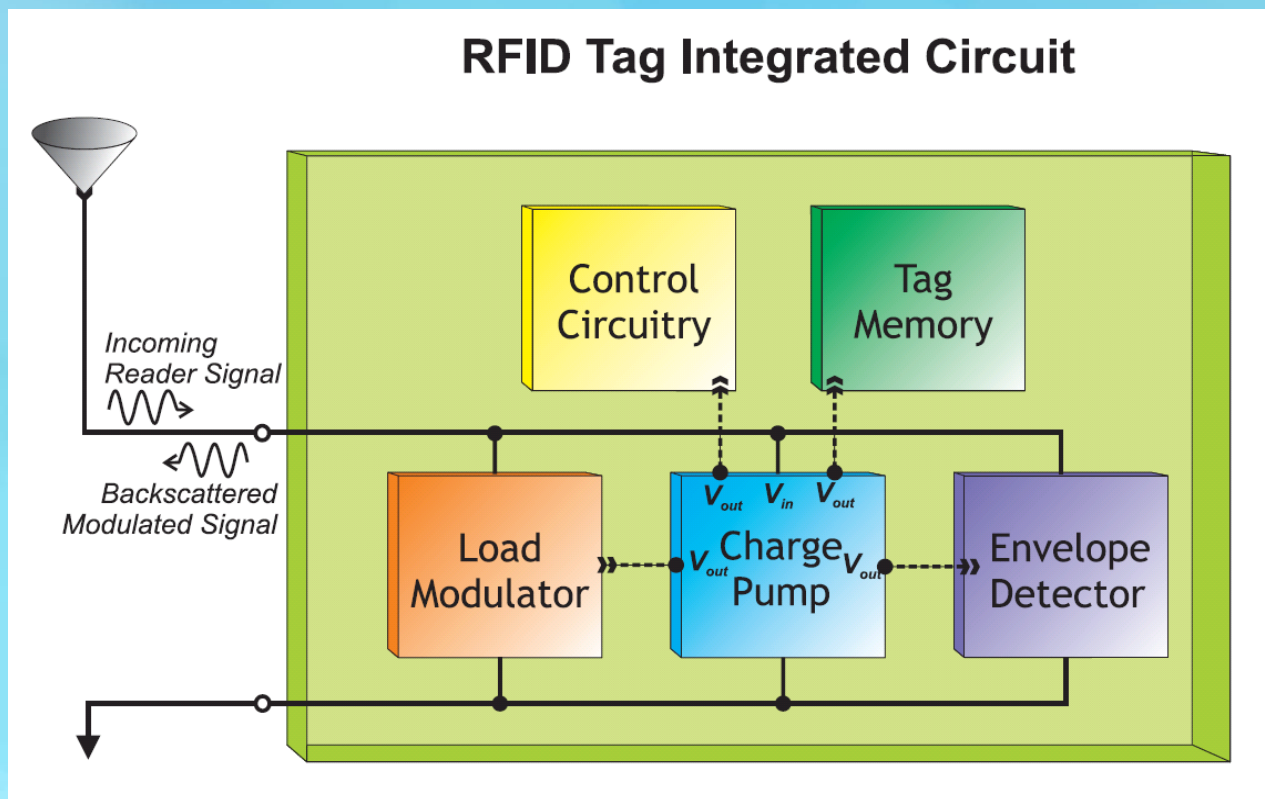

M.S. Trotter, J.D. Griffin, and G.D. Durgin. "Power-Optimized Waveforms for Improving the Range and Reliability of RFID Systems." *IEEE RFID 09 Conference*, Orlando, FL. April 2009. 8 pages.

Greg Durgin

Energy Harvesting

Historical Power-Up for UHF RFID


- Uses “Goldilocks” link assumptions
 - Maximum unlicensed EIRP
 - No blockages, fading
 - Dipole tag antenna, floating in space
 - No polarization mismatch
- Innovation lowers “turn-on” power
 - Smaller integration size
 - Power-stingy circuitry
 - Antenna design and matching
 - Charge management systems
- Fundamental limit imposed by conventional CMOS processes that convert CW RF ... *and we’re there!*

G. D. Durgin, "RF thermoelectric generation for passive RFID," 2016 IEEE International Conference on RFID (RFID), Orlando, FL, USA, 2016, pp. 1-8

IEEE
RFID
2026

Greg Durgin

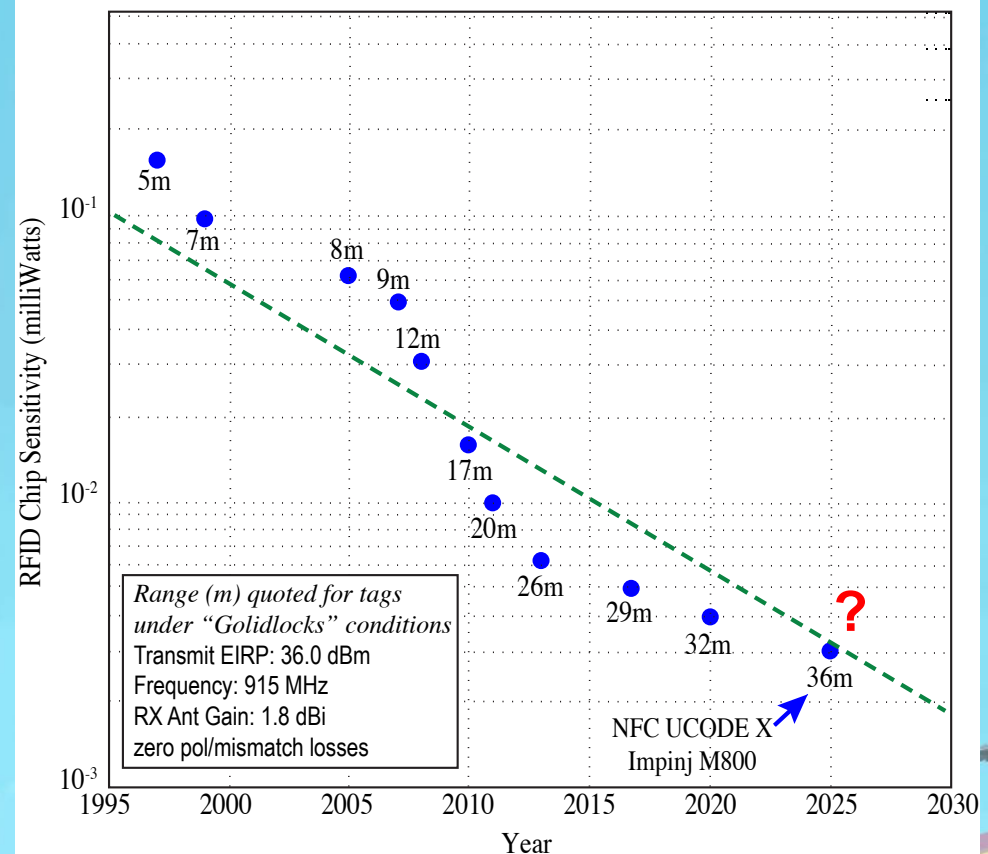Passive UHF RFID Chip Sensitivity Over The Years



IEEE
RFID

What Comes Out of an Antenna?

IEEE
RFID
2026

Greg Durgin

Energy Harvesting



Antenna Matching

$$P_T = \underbrace{\frac{4R_S R_A}{|\tilde{Z}_S + \tilde{Z}_A|^2}}_{\text{mismatch losses}} P_S$$


Not all of the source power transmits

$$P_R = \frac{V_A'^2}{8R_A}$$

This is the received power at RX antenna

$$V_A = |\tilde{V}_A| = \frac{2|\tilde{Z}_L| \sqrt{2R_A P_R}}{|\tilde{Z}_A + \tilde{Z}_L|}$$

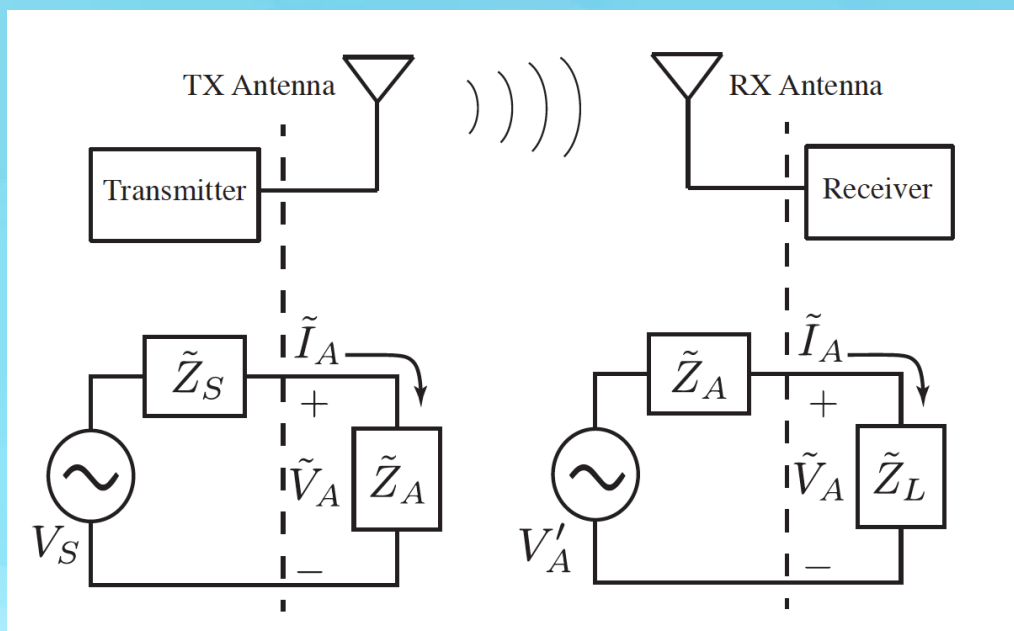For energy-harvesting, you also need to check the voltage amplitude



$$P_L = \underbrace{\frac{4R_L R_A}{|\tilde{Z}_A + \tilde{Z}_L|^2}}_{\text{mismatch losses}} P_R$$

Not all of the received power makes it into the load



Example UHF RFID Tag

- Electrically shortened half-wave dipole
- Radiation path is meandered to lower terminal capacitance at the IC
- Electrical “ballast” at the ends to add electrical length and bandwidth
- Inductive coupling loop added to boost real impedance and reactive component
- Radiation pattern is the same as nearly all other short UHF tags




Alien UHF RFID Squiggle Tag

Enemy of UHF Power Transfer: Everything

Detrimental Effects When Tags Placed on Objects

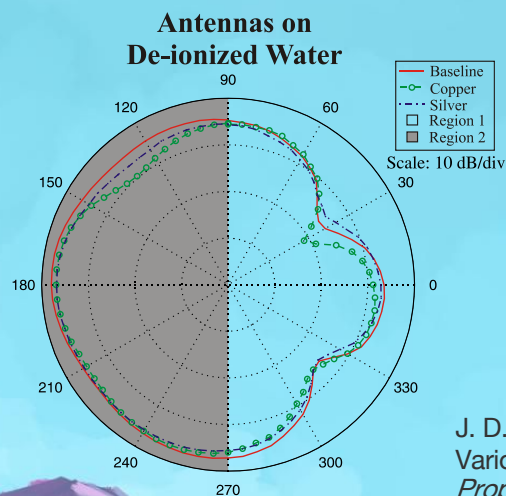- Gain Penalty to the Radiation
- "Pattern Sucking"
- Highly Mismatched Circuit





	AGP (dB)	ϵ_r	$\tan \delta$
Cardboard Sheet	0.9	≈ 1	≈ 0
Acrylic Slab	1.1	2.6	0.0061
Pine Plywood	4.7	1.7	0.036
De-ionized Water	5.7	77.3	0.048
Ethylene Glycol**	7.4	33	0.4
Ground Beef***	7.4	50	0.7
Aluminum Slab	9.4	-	-

J. D. Griffin, G. D. Durgin, A. Haldi and B. Kippelen, "RF Tag Antenna Performance on Various Materials Using Radio Link Budgets," in *IEEE Antennas and Wireless Propagation Letters*, vol. 5, pp. 247-250, 2006




Near-Field Excitation

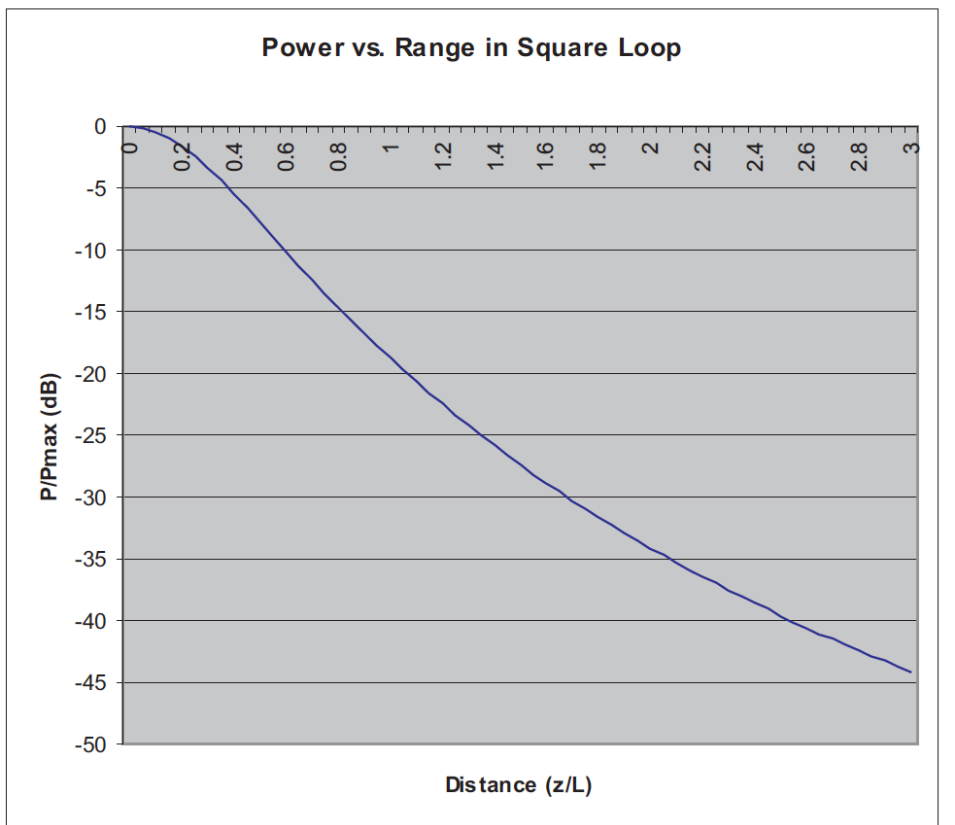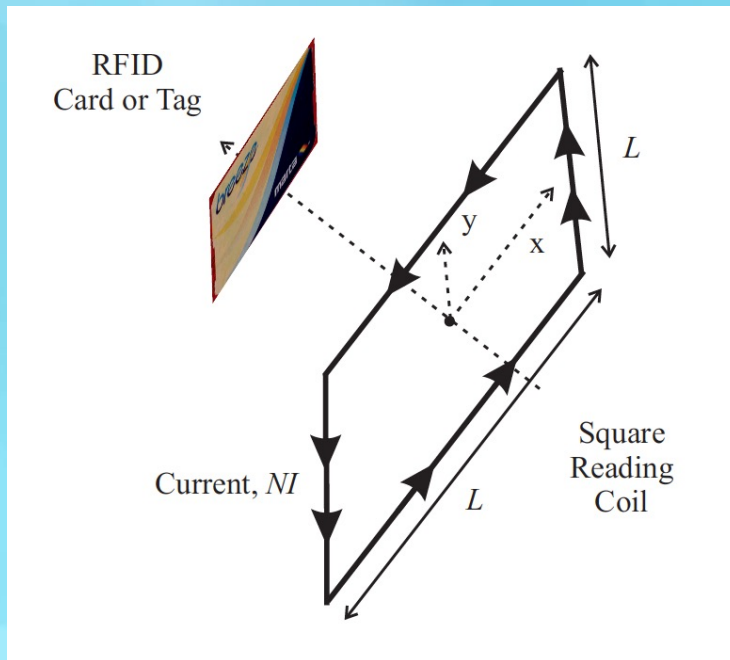

Separation distance: $r \ll \lambda$

Magnetic Field Modeling of a Pick-up Coil

Magnetic Field Cross-Section

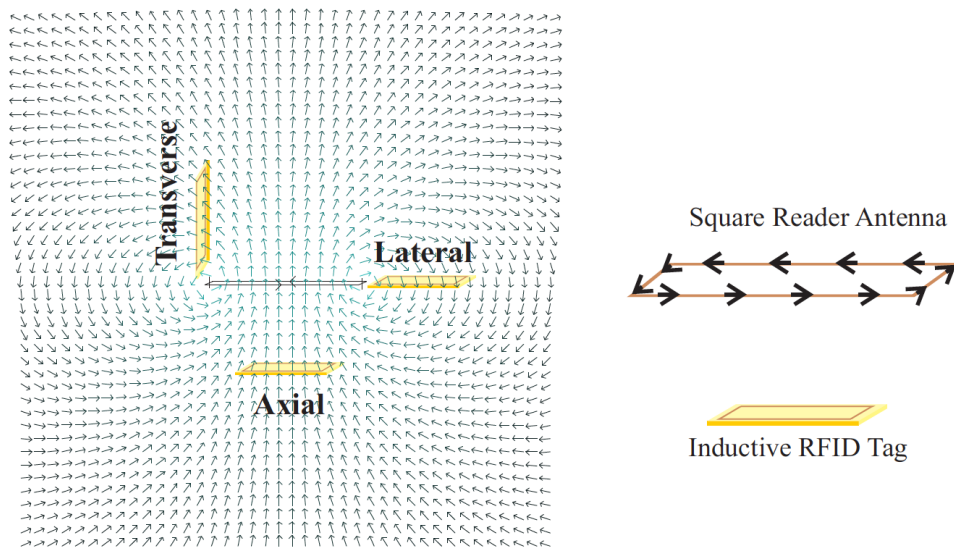


Three Modes of Inductive Wireless Power Transfer

- Axial
- Lateral
- Transverse


Anatomy of HF RFID

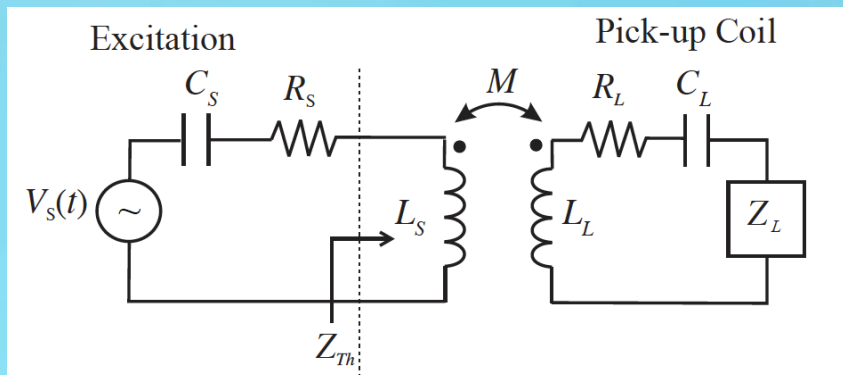How to make an HF energy-harvesting circuit




Inductive Load Thevenin Equivalent
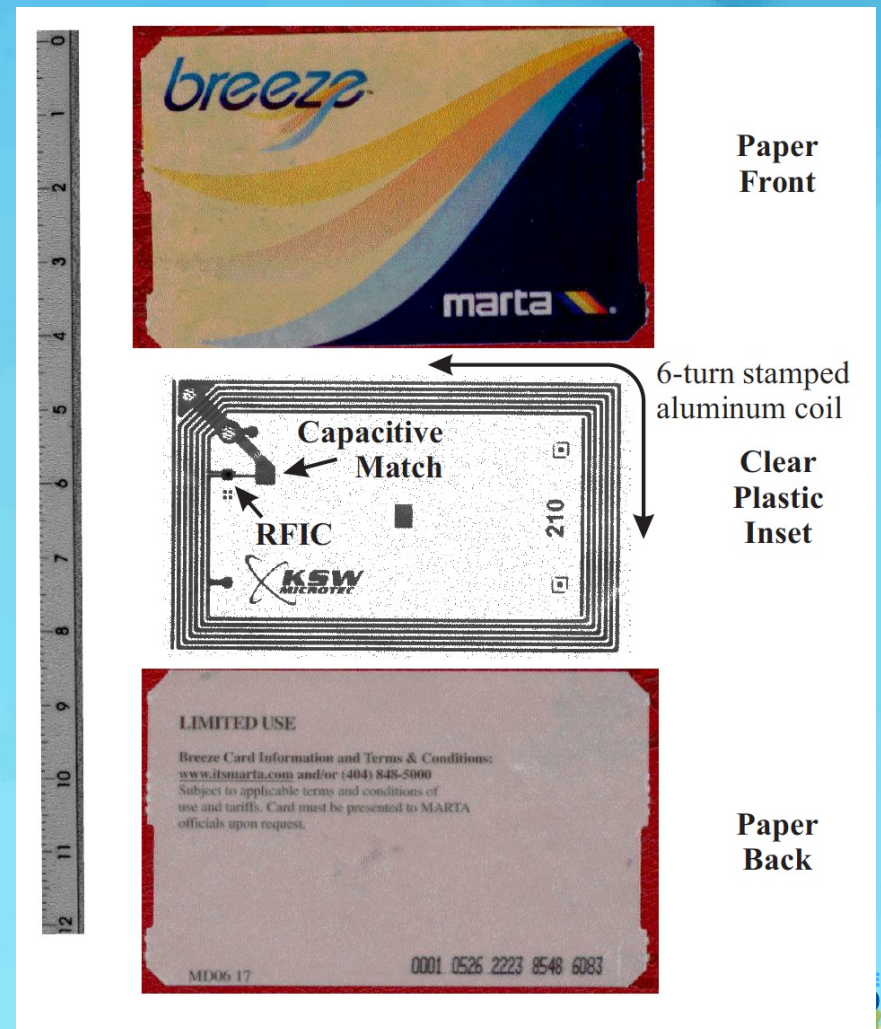
$$\tilde{Z}_{th} = j2\pi f L_S + \frac{4\pi^2 f^2 M^2}{R_L + j2\pi f L_L - \frac{j}{2\pi f C_L} + \tilde{Z}_L}$$




Enemy of Inductive Power Transfer: Metal

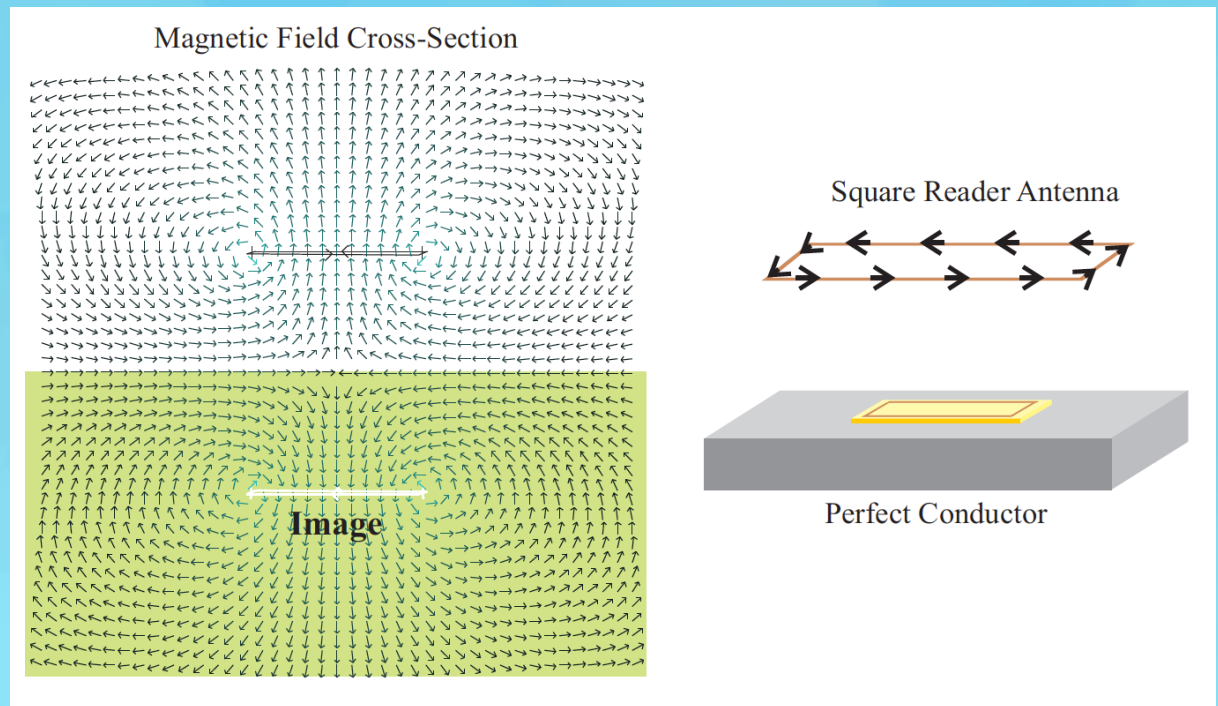- Eddy/Image currents do not allow perpendicular fields near metal
- Leads to bad impedance mismatch *and* drop in mutual coupling between tag and reader



AutoTune in RFID Tags and Power Transfer

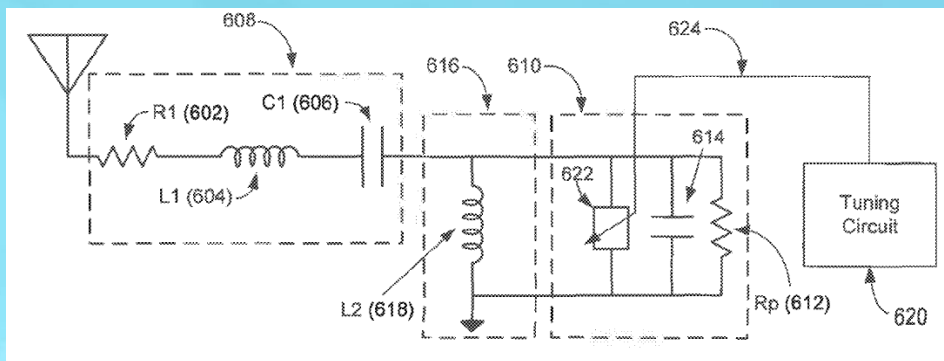- Auto-tune circuit powers on before the rest of RFID tag's state machines
- Used in HF and UHF tags
- Circuit switches in different RF capacitors until maximum power achieved



US009471816B1

(12) **United States Patent**
Hyde et al.

(10) **Patent No.:** **US 9,471,816 B1**
(45) **Date of Patent:** **Oct. 18, 2016**

(54) **INCREASING DYNAMIC RANGE OF RFID TAG SELF-TUNING**

(71) Applicant: **Impinj, Inc.**, Seattle, WA (US)

(72) Inventors: **John Hyde**, Corvallis, OR (US);
Theron Stanford, Seattle, WA (US);
Harley Heinrich, Snohomish, WA (US);
Omer Onen, Redmond, WA (US);
Charles Peach, Kirkland, WA (US)

(73) Assignee: **IMPINJ, INC.**, Seattle, WA (US)

(*) Notice: Subject to any disclaimer, the term of this patent is extended or adjusted under 35 U.S.C. 154(b) by 0 days.

(21) Appl. No.: **14/711,717**

(22) Filed: **May 13, 2015**

G06K 19/073; G06K 19/0775; G06K 19/07745; G06K 19/0775; G06K 7/10297; G06K 7/10158; G06K 19/0723
USPC 340/10.5, 10.34, 10.1, 10.6, 334, 572; 235/492, 488; 438/26
See application file for complete search history.

(56)

References Cited

U.S. PATENT DOCUMENTS

8,952,792 B1 * 2/2015 Srinivas H01Q 1/2208 340/10.1
2014/0070010 A1 * 3/2014 Diorio G06K 19/0773 235/492
2014/0073071 A1 * 3/2014 Diorio G06K 19/0723 438/26
2014/0144992 A1 * 5/2014 Diorio G06K 7/10297 235/488
2015/0227832 A1 * 8/2015 Diorio G06K 19/07745 235/492

* cited by examiner



Converting RF to DC

IEEE
RFID
2026

Greg Durgin


Energy Harvesting




How to Rectify RF

- RF is just a high-frequency form of alternating current
- But we need DC voltage to drive memory, logic, sensing, etc.
- Need a nonlinear circuit to passively “change” frequencies (by definition)

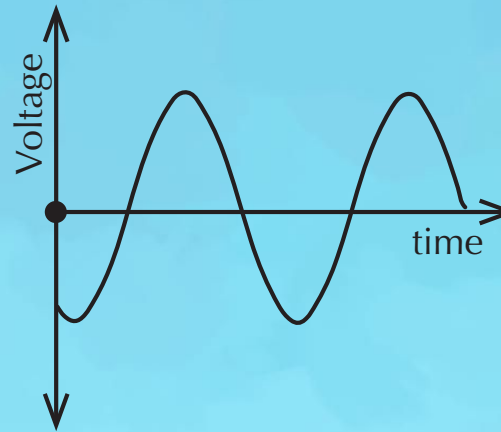Alternating Current (AC)
or Radio Frequency (RF)
Waveform




Direct Current (DC)
Waveform

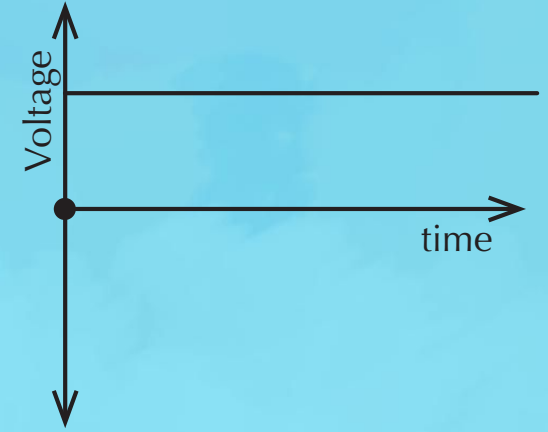


Half-Wave Rectifier

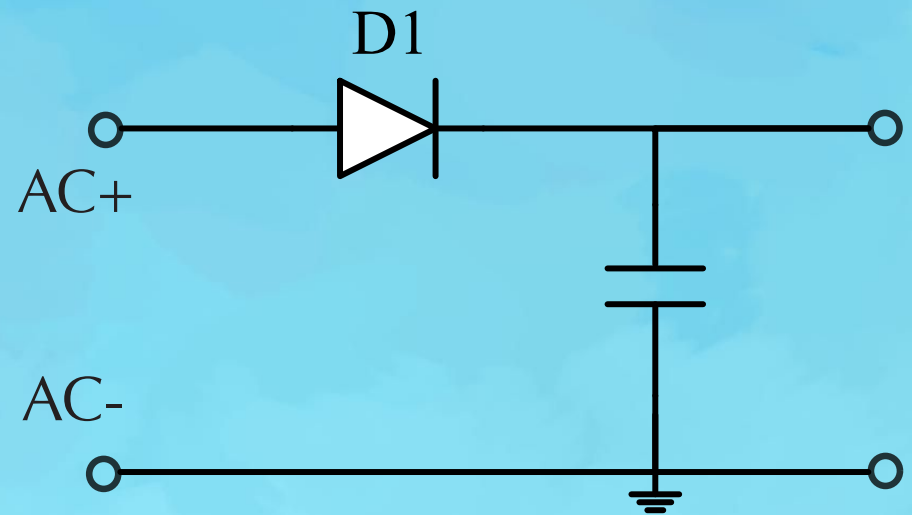- Half-wave rectifier for RF-to-DC conversion
- Similar circuit is also used as a detector
- Extremely simple design
- Only converts on one cycle of the RF waveform




Half-Wave Rectifier Operation


Operation of a
Half-Wave
Rectifier

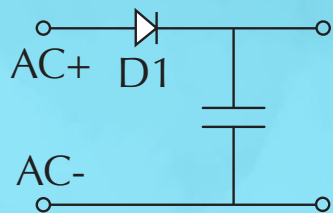

RF Input Voltage
(positive swing)

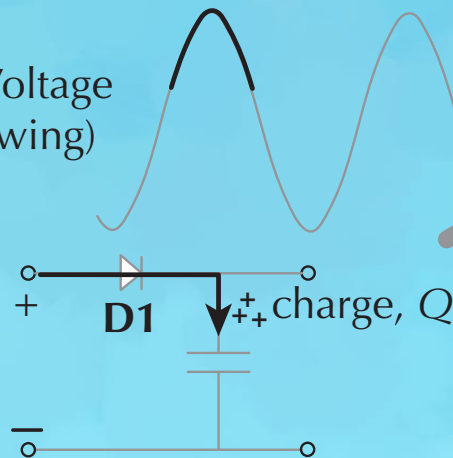


RF Input Voltage
(negative swing)

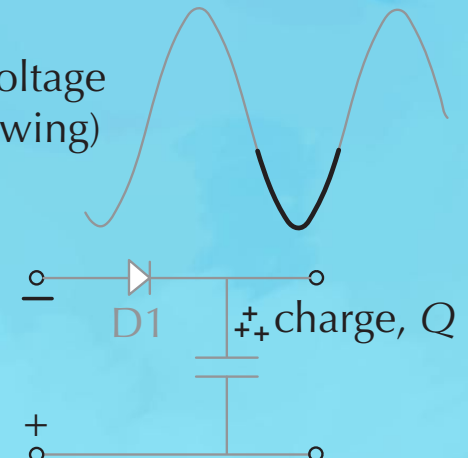


Bridge Rectifier

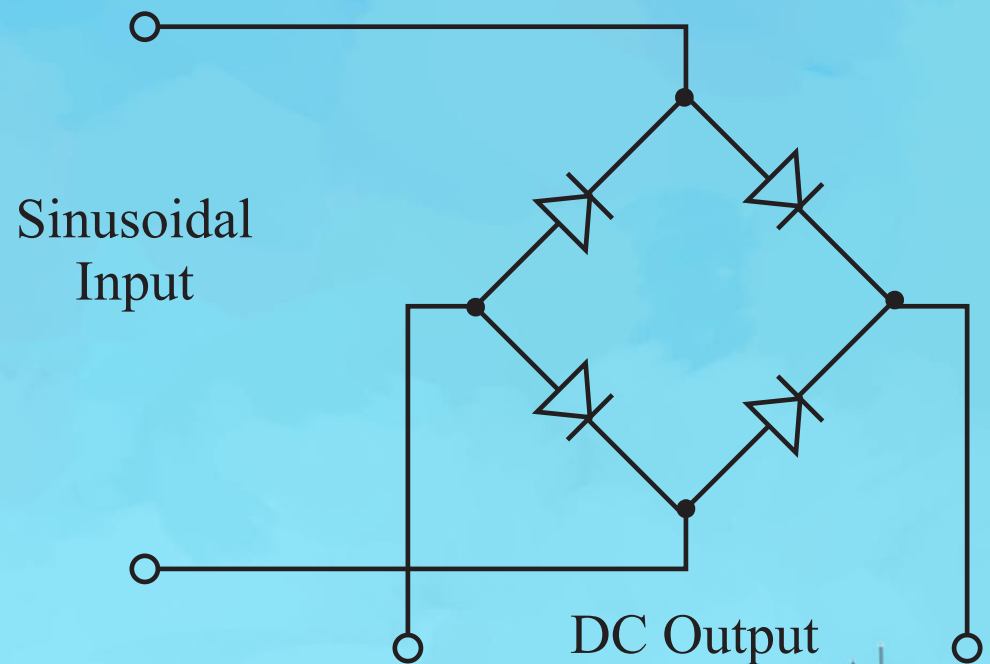- Used in AC-to-DC power conversion
- Useful because there are no capacitors (except at the output to smooth ripple on the DC supply)
- Full-wave rectification
- Less useful for RF because it requires turning on two diodes per cycle (loss of conversion efficiency at low levels)




Bridge Rectifier Operation


Operation of a Bridge Rectifying Stage

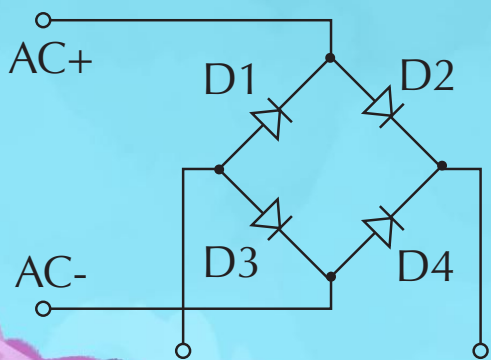

RF Input Voltage (positive swing)

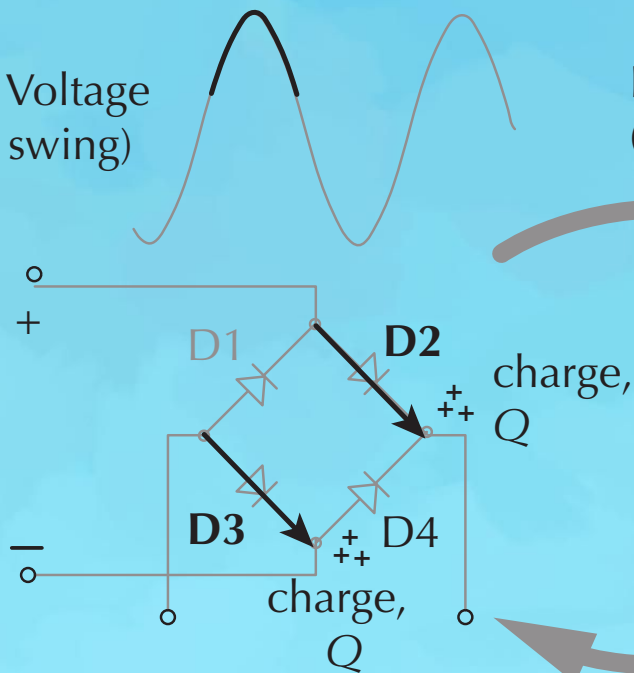


RF Input Voltage (negative swing)

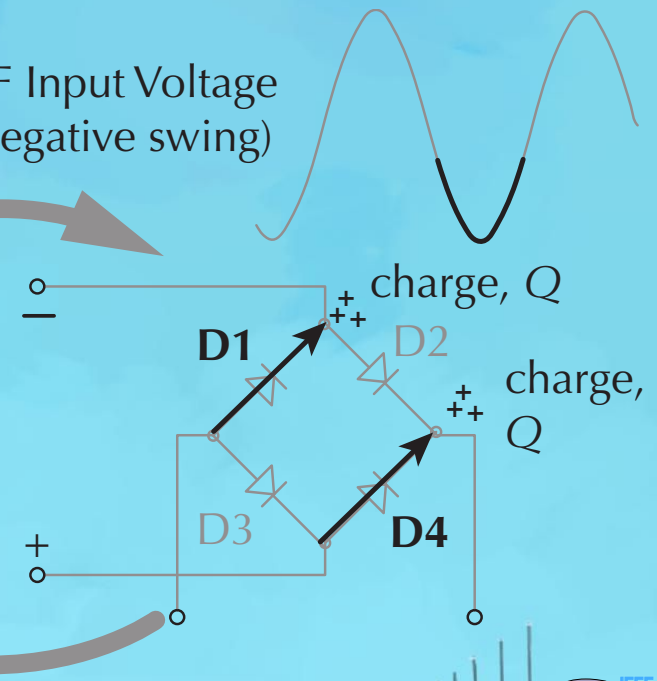


Full-Wave Rectifier/Doubler

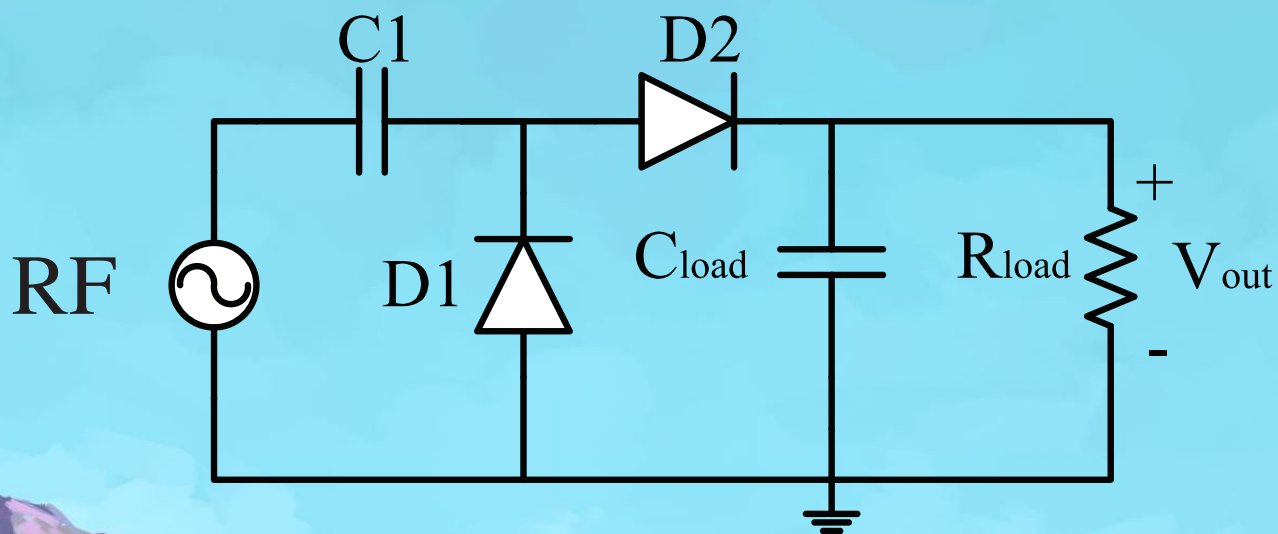- Two capacitors and diodes
- Arranged to *double* DC voltage at the output (often called a voltage doubler)
- Only one diode needs to turn on at a time




Full Wave Rectifier/Doubler Operation


Operation of a
Full-Wave
Rectifier

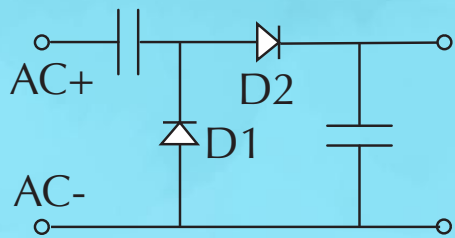

RF Input Voltage
(positive swing)

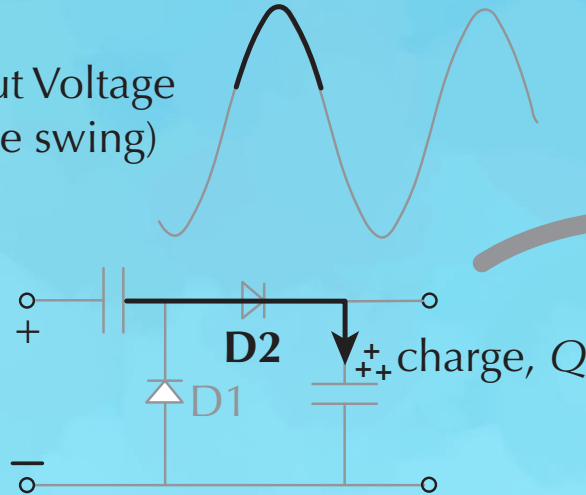

RF Input Voltage
(negative swing)

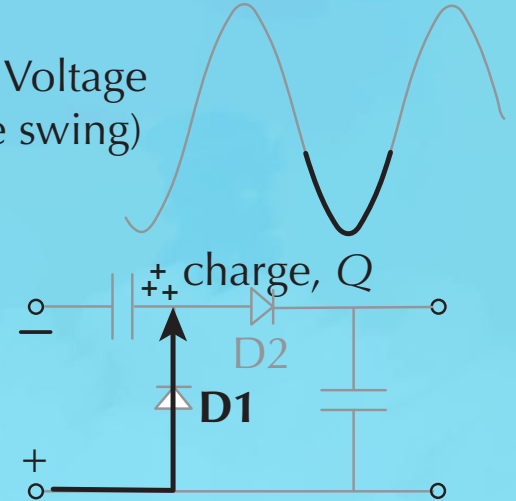

It's Actually Easy to Build a Diode Rectifier

- Thomas and Degnan showed that you can even do it by accident!
- Right is diagram of a microcontroller pin with electrostatic discharge (ESD) diodes and capacitors that behave like RF rectifiers

S. J. Thomas, B. P. Degnan, C. Callupe Chavez and B. Culver, "Backscatter Ex-Nihilo: Single-component, Fully-passive Backscattering for Microcontrollers," 2020 IEEE International Conference on RFID (RFID), Orlando, FL, USA, 2020


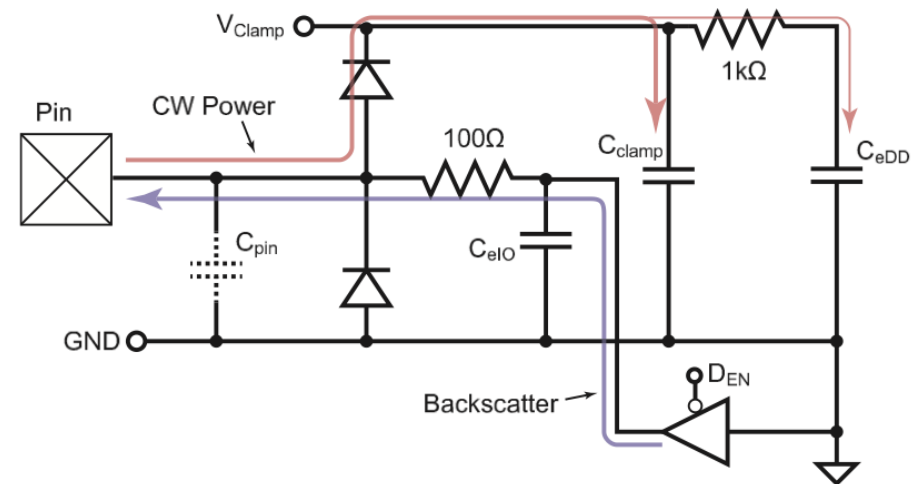
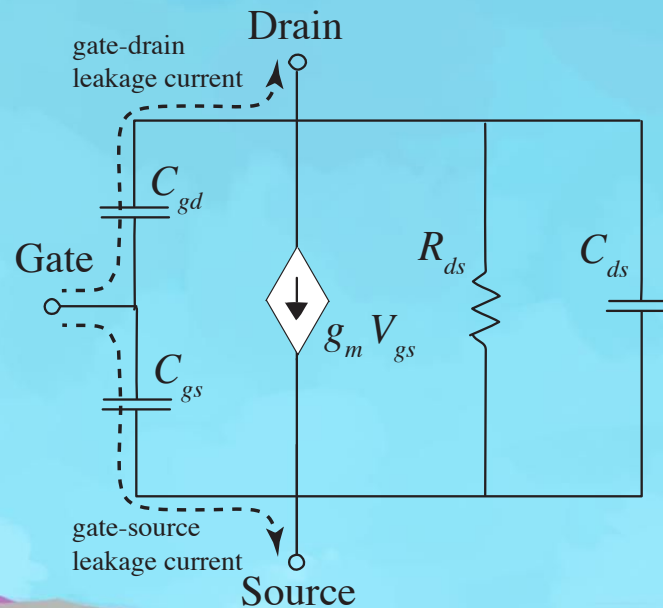


Fig. 4. The illustration depicts a simplified ESD structure where an ESD diode is used to place charge on capacitor. The GPIO driver enable line is then used as a backscatter load.


The Problem With Diodes

- RF transmissions nearly always produce low voltages at the output of the antenna
- Thus, lower RF levels convert at lower efficiencies
- This is a fundamental limit of *any* conversion circuitry (PN diodes, Schottky diodes, CMOS diodes, etc.)

MOSFET Circuit Element

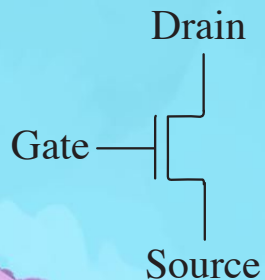


Diode-Connected MOSFET

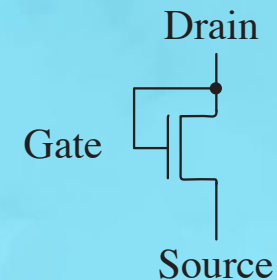


Charge Pumps

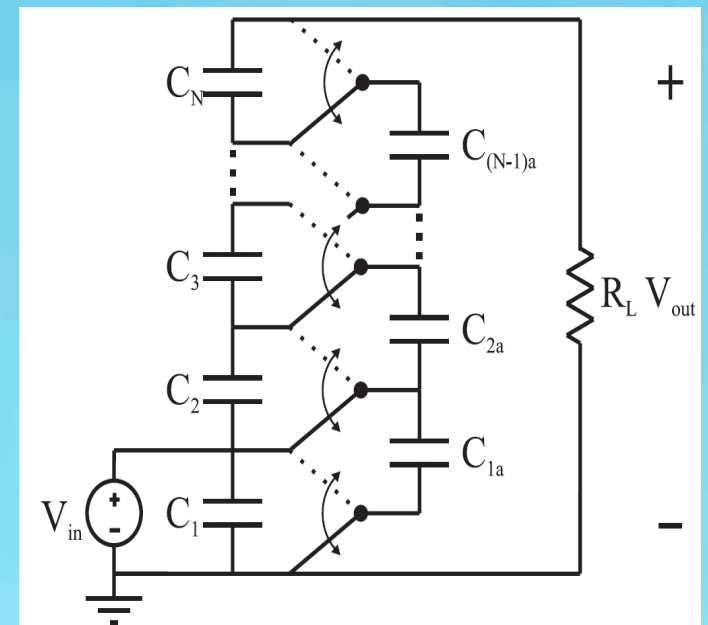- Cockcroft-Walton multiplier (1932)
 - Only uses capacitors
 - Also requires mechanical switching
- Part of Nobel Prize-winning work on splitting atom
- Required large voltages for their particle accelerator
- Still used today




Multi-Stage Rectifier Circuit

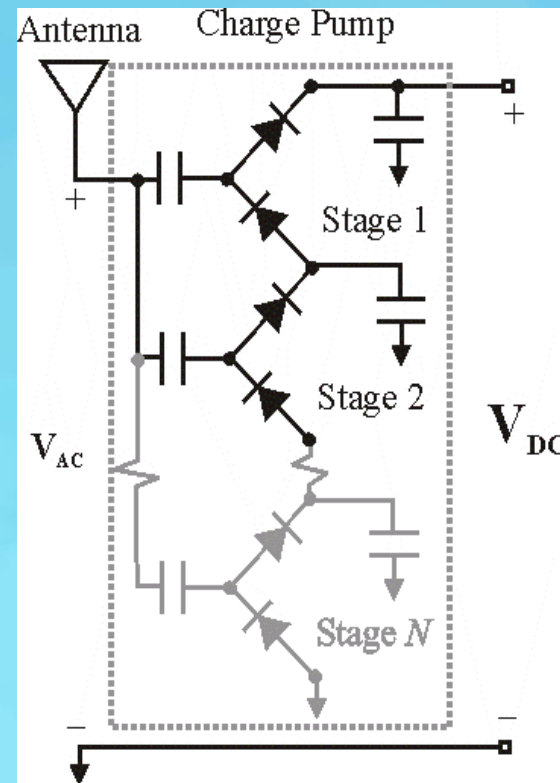- Charge pump rectifier
 - Diodes and capacitors
 - AC voltage converted to DC
 - Voltage stepped up (current stepped down)
- Ideal Voltage Conversion:
$$V_{DC} = N(V_{AC})_{pp} - 2NV_{T0}$$
- Drawbacks
 - Higher complexity
 - Diminishing returns for added stages
 - Longer charging transient




Single Shunt Rectifier

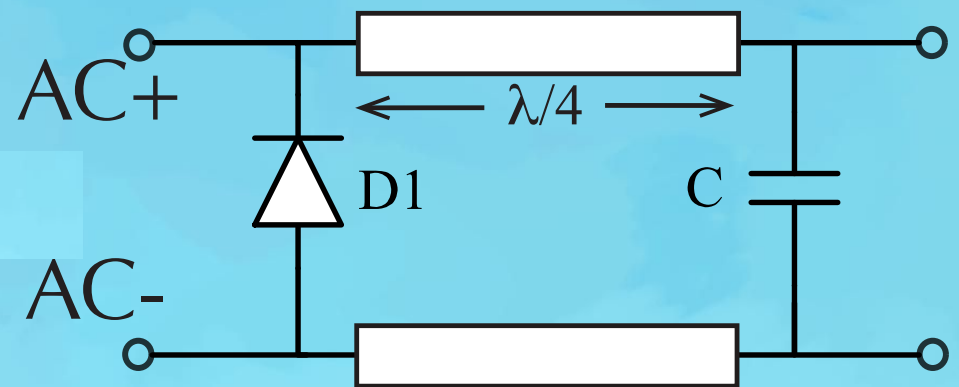
- Single diode+cap and quarter-wave transformer line
- Only one turn-on voltage, but full-wave rectification
- Useful for IoT devices on circuit boards





Single-Shunt Rectifier Operation

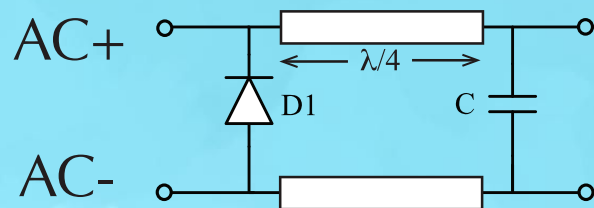


RF Input Voltage
(positive swing)

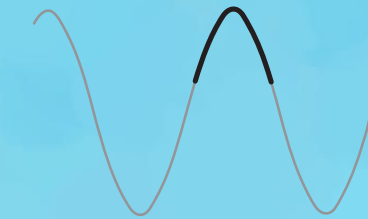


RF Input Voltage
(negative swing)

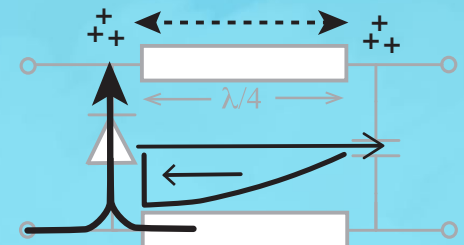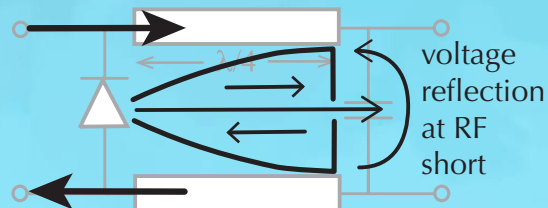


And the Rest...

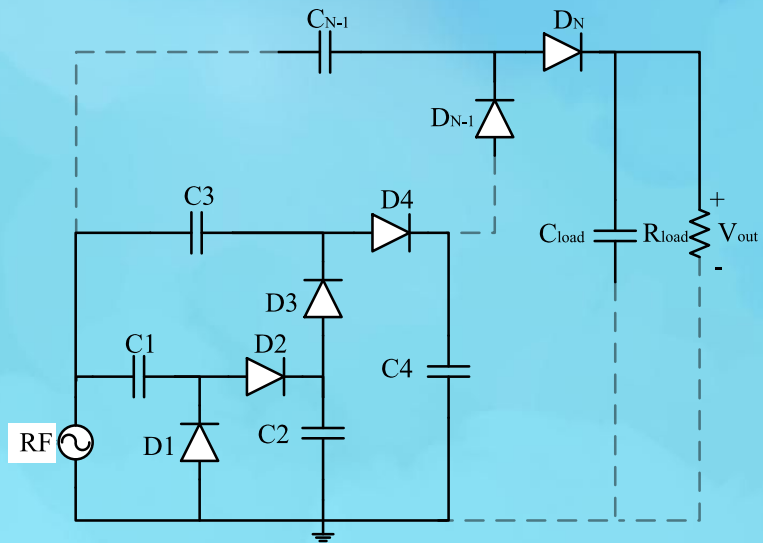


Dickson Charge Pump

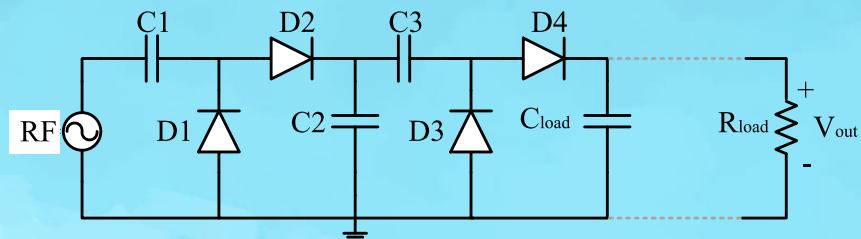

N-Voltage Multiplier

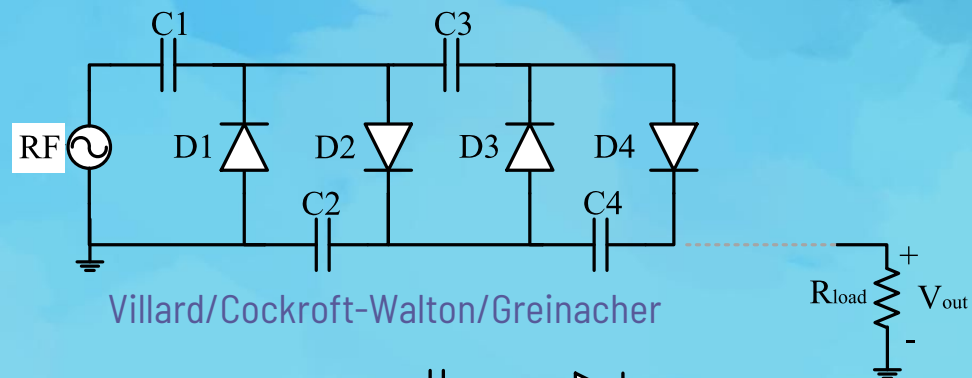

Villard/Cockroft-Walton/Greiner

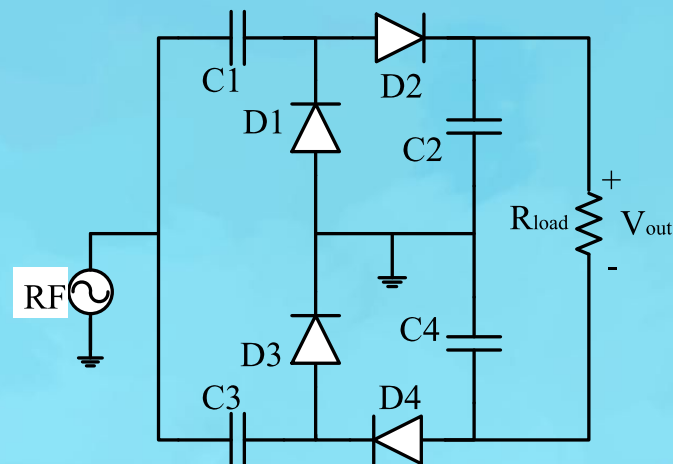

Modified Cockroft-Walton/Greiner

Conversion Efficiency

IEEE
RFID
2026


Greg Durgin

Energy Harvesting




Diode Efficiency

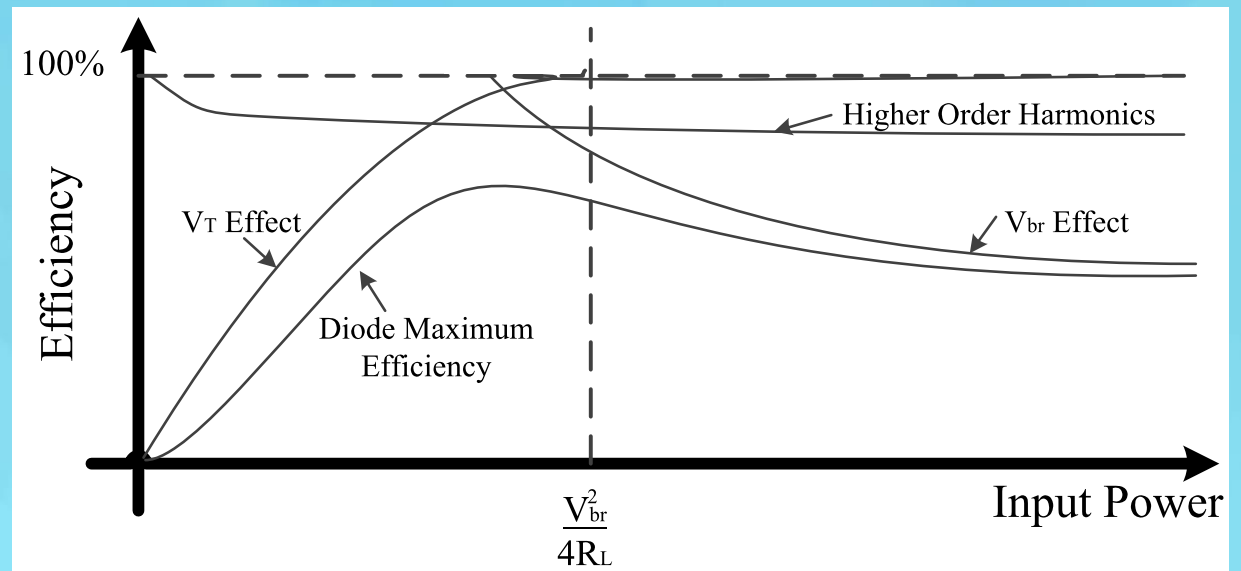- Harmonics and other inefficiencies (all powers)
- Losses due to the diode/transistor turn-on effect (low-power)
- Reverse breakdown of diodes (high-power)



C. R. Valenta and G. D. Durgin, "Harvesting Wireless Power: Survey of Energy-Harvester Conversion Efficiency in Far-Field, Wireless Power Transfer Systems," in *IEEE Microwave Magazine*, vol. 15, no. 4, pp. 108-120, June 2014

The Valenta Diagram

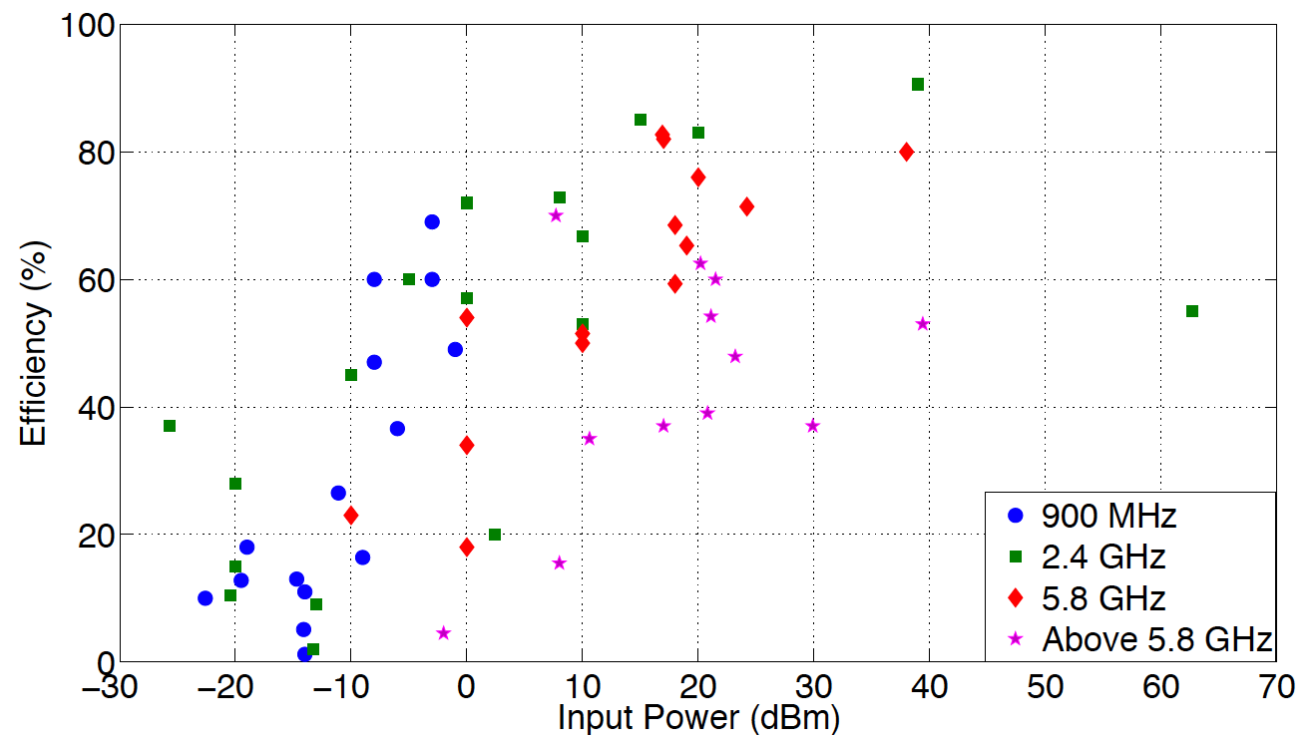

Christopher Valenta
GTRI


C. R. Valenta and G. D. Durgin, "Harvesting Wireless Power: Survey of Energy-Harvester Conversion Efficiency in Far-Field, Wireless Power Transfer Systems," in *IEEE Microwave Magazine*, vol. 15, no. 4, pp. 108-120, June 2014



Power Optimized Waveforms



Matthew Trotter
Georgia Tech

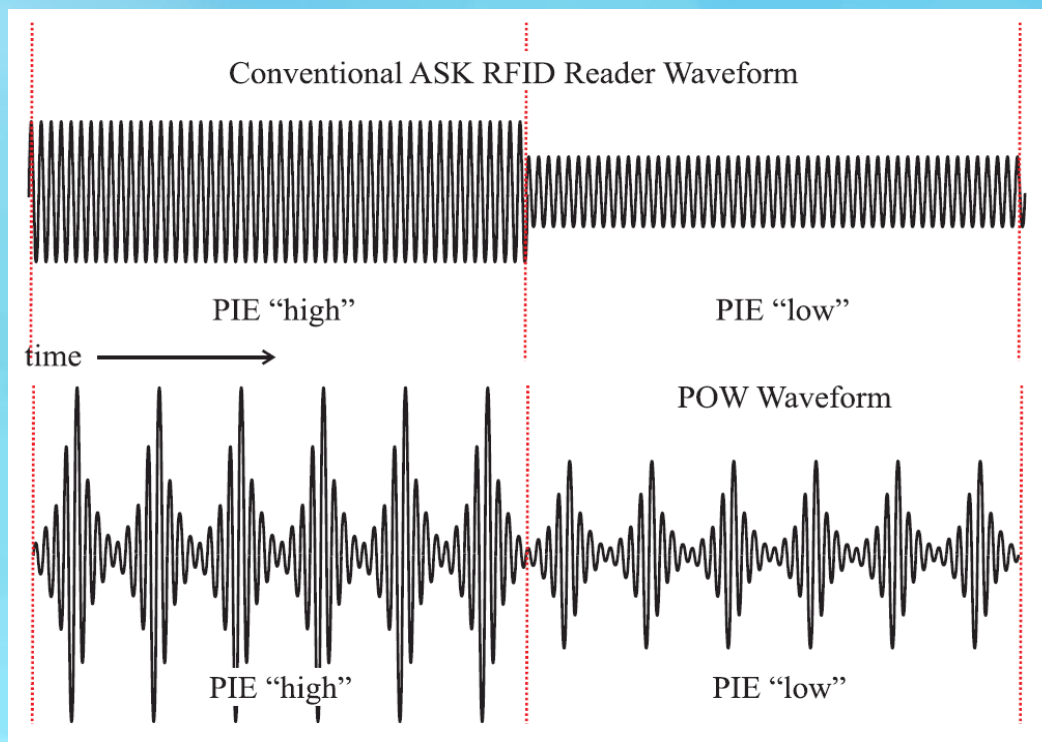

M. S. Trotter, J. D. Griffin and G. D. Durgin, "Power-optimized waveforms for improving the range and reliability of RFID systems," *2009 IEEE International Conference on RFID*, Orlando, FL, USA, 2009, pp. 80-87



Now Let's Do It In CMOS!

IEEE
RFID
2026


Greg Durgin

Energy Harvesting




Complimentary Metal Oxide Semiconductor Si Transistors


n-MOSFET
Circuit Element

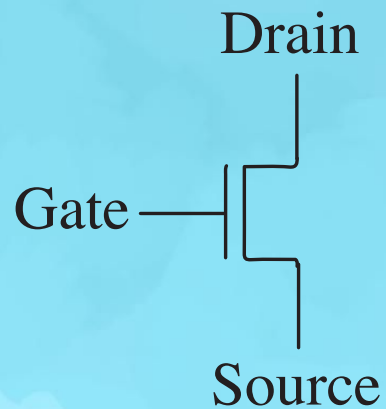

p-MOSFET
Circuit Element

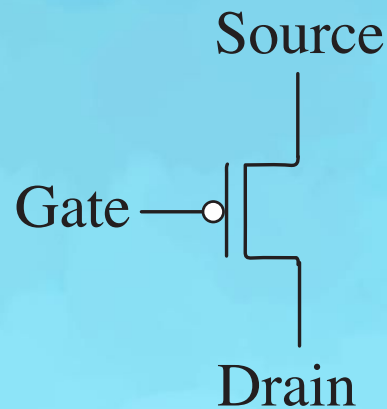

CMOS
Inverter

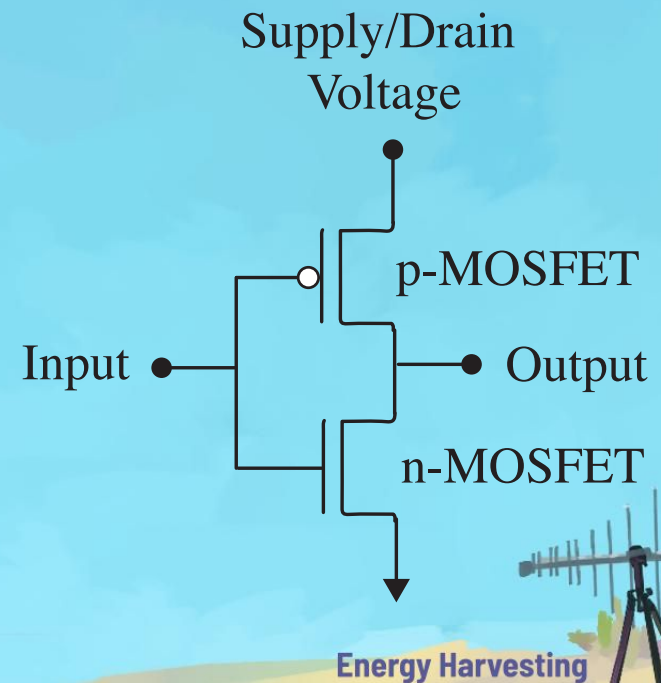

Mandal Charge Pump

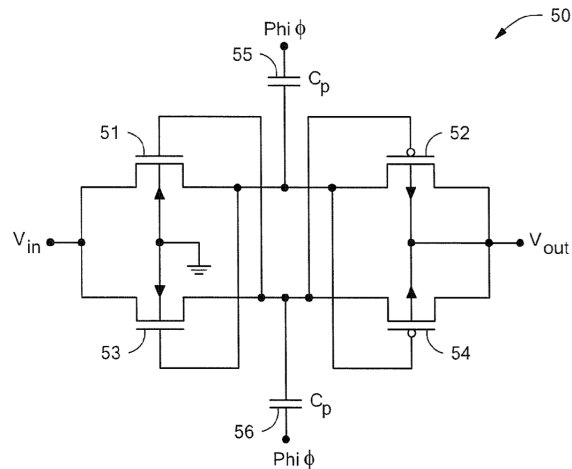


FIG. 8

- 4-transistor, Repeatable Unit
- Self-biasing unit (DC on gates to optimize)
- Simple, Elegant



US008045947B2

(12) **United States Patent**
Mandal et al.

(10) **Patent No.:** **US 8,045,947 B2**
(45) **Date of Patent:** ***Oct. 25, 2011**

(54) RF POWER EXTRACTING CIRCUIT AND RELATED TECHNIQUES

(75) Inventors: **Soumyajit Mandal**, Cambridge, MA (US); **Rahul Sarpeshkar**, Arlington, MA (US)

(73) Assignee: **Massachusetts Institute of Technology,**
Cambridge, MA (US)

(*) Notice: Subject to any disclaimer, the term of this patent is extended or adjusted under 35 U.S.C. 154(b) by 909 days.

This patent is subject to a ten-year non-competition claimer.

(21) Appl. No.: 11/609,060

(22) Filed: **Dec. 11, 2006**

(65) **Prior Publication Data**

US 2007/0087719 A1 Apr. 19, 2007

4,360,741	A *	11/1982	Fitzsimmons et al.	307/151
4,706,182	A *	11/1987	Masuda	363/139
5,870,031	A *	2/1999	Kaiser et al.	340/10.34
5,920,129	A *	7/1999	Smith	307/64
6,008,508	A *	12/1999	Bergemont et al.	257/175
6,140,924	A *	10/2000	Chia et al.	340/572.5
6,212,431	B1	4/2001	Hahn et al.	
6,271,796	B1 *	8/2001	Itoh et al.	343/702
6,346,922	B1 *	2/2002	Proctor et al.	343/795
6,400,274	B1	6/2002	Duan et al.	
6,486,776	B1	11/2002	Pollack et al.	
6,639,459	B1	10/2003	Devilbiss	
6,693,599	B1	2/2004	Chia et al.	
2003/0102961	A1	6/2003	Fischer et al.	
2005/0082636	A1	4/2005	Yashima et al.	
2006/0102961	A *	2/2006	Oliver et al.	340/572.4

T DOCUMENTS
5/2003

—Daly, Crowley, Mofford &




Soumyajit Mandal 
MIT/Brookhaven National Labs

Energy Harvesting




Mandal Charge Pump Operation

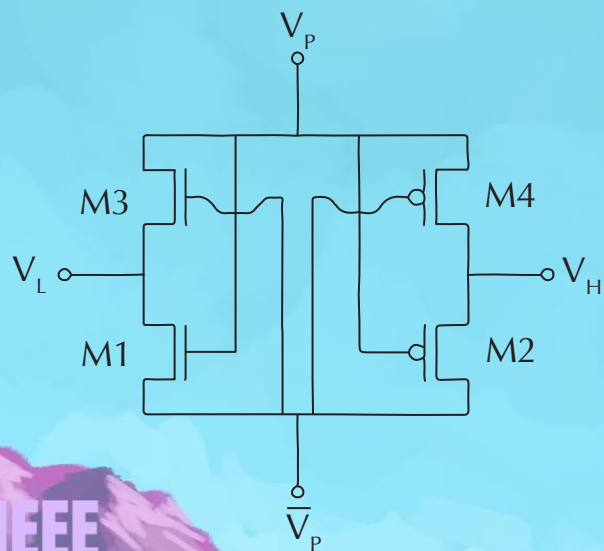
Operation of a
Four-Transistor CMOS
Rectifying Stage



RF Input Voltage
(positive swing)

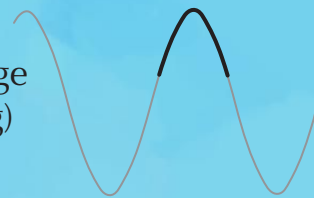


RF Input Voltage
(negative swing)

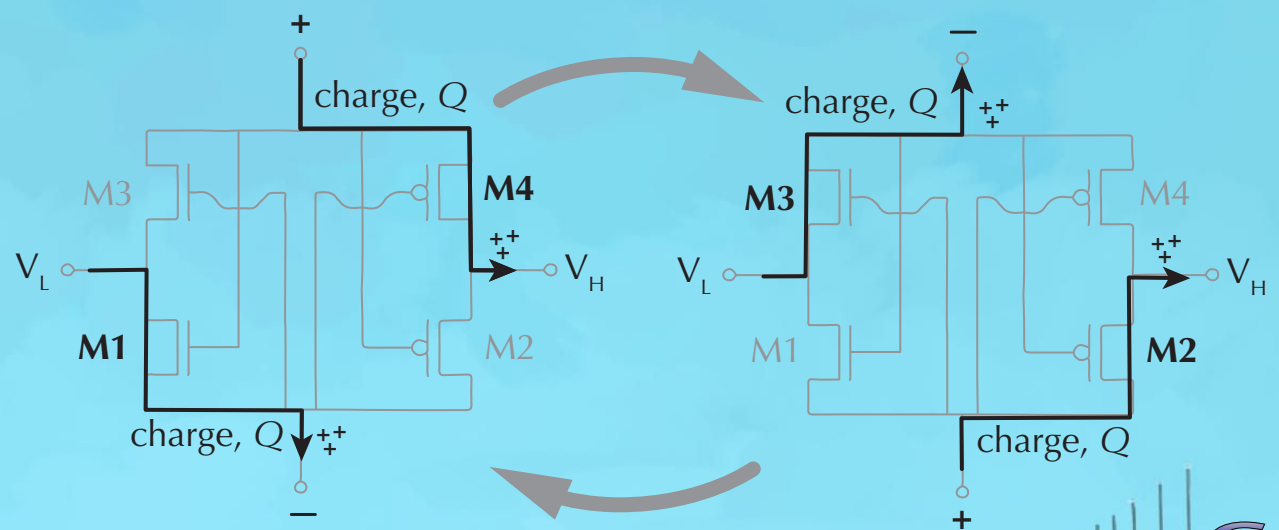


Multiple Stages

Operation of a Multi-stage
Four-Transistor Rectifier

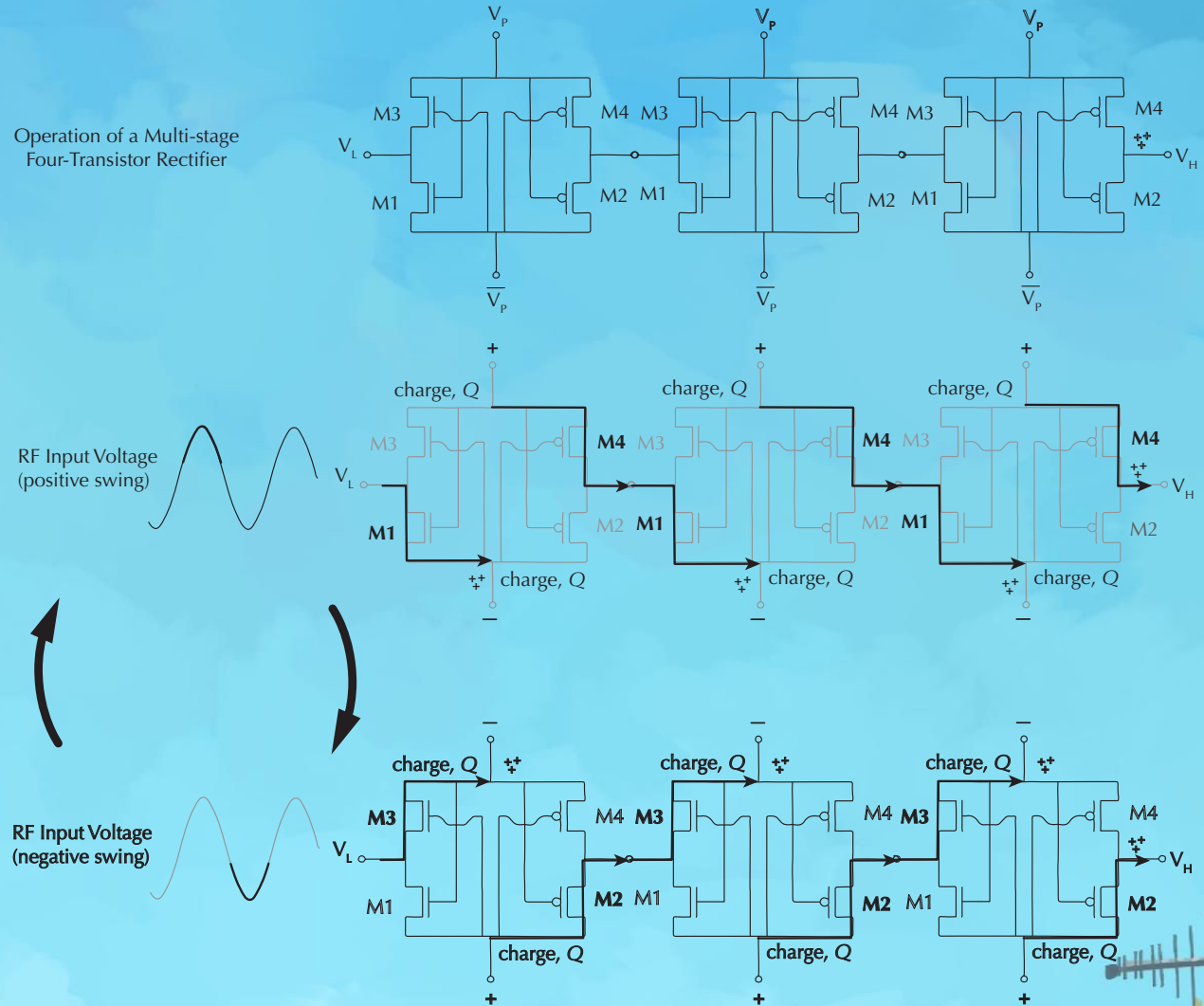Mandel Charge
Pumps can be
connected in series
to boost DC voltage



Oliver Charge Pump

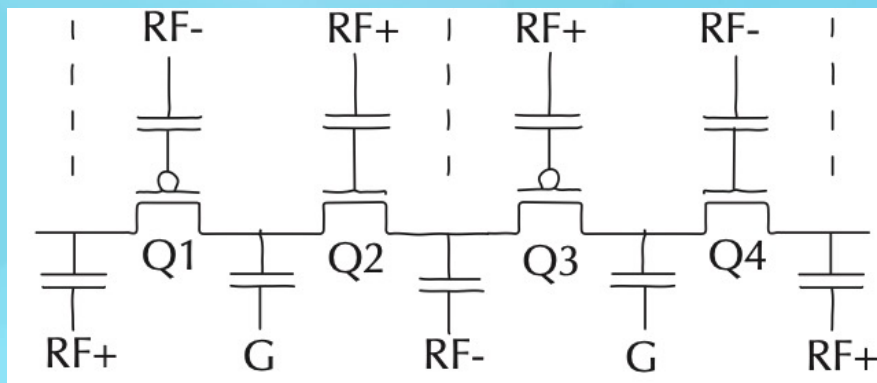

- Series Pair of 2-transistor, Repeatable Unit
- Draws Less Current from Antenna
- Does not self-bias

IEEE
RFID
2026

Greg Durgin




US008115597B1

(12) **United States Patent**
Oliver et al.

(10) **Patent No.:** **US 8,115,597 B1**
(45) **Date of Patent:** **Feb. 14, 2012**

- (54) **RFID TAGS WITH SYNCHRONOUS POWER RECTIFIER**
- (75) Inventors: **Ronald A. Oliver**, Seattle, WA (US);
John D. Hyde, Corvallis, OR (US);
Charles J. T. Peach, Seattle, WA (US)
- (73) Assignee: **Impinj, Inc.**, Seattle, WA (US)
- (*) Notice: Subject to any disclaimer, the term of this patent is extended or adjusted under 35 U.S.C. 154(b) by 1012 days.
- (21) Appl. No.: **12/042,117**
- (22) Filed: **Mar. 4, 2008**
- Related U.S. Application Data**
- (60) Provisional application No. 60/905,417, 2007.
- | | | | |
|----------------|---------|----------------------|------------|
| 4,032,838 A * | 6/1977 | Minami et al. | 323/349 |
| 5,394,367 A | 2/1995 | Downs et al. | |
| 5,467,081 A | 11/1995 | Drews et al. | |
| 5,535,164 A | 7/1996 | Adams et al. | |
| 5,606,323 A * | 2/1997 | Heinrich et al. | 340/10.34 |
| 5,630,216 A * | 5/1997 | McEwan | 455/215 |
| 5,659,502 A * | 8/1997 | Sali et al. | 365/185.18 |
| 5,874,896 A * | 2/1999 | Lowe et al. | 340/572.1 |
| 5,936,454 A * | 8/1999 | Joardar | 327/432 |
| 6,023,188 A * | 2/2000 | Lee et al. | 327/536 |
| 6,040,773 A * | 3/2000 | Vega et al. | 340/572.1 |
| 6,147,605 A * | 11/2000 | Vega et al. | 340/572.7 |
| 6,154,014 A * | 11/2000 | Suu | 323/222 |
| 6,252,508 B1 * | 6/2001 | Vega et al. | 340/572.1 |
| 6,297,974 B1 * | 10/2001 | Ganesan et al. | 363/60 |
| 6,320,230 B1 * | 11/2001 | Yu | 257/355 |
| 6,496,112 B1 * | 12/2002 | Vega | 340/572.1 |
| 6,753,704 B2 * | 6/2004 | Desgrez et al. | 327/9 |
| | | Vatanabe et al. | 327/359 |
- (continued)
- REFERENCES**
- RFID Air Interface-EPC Radio-

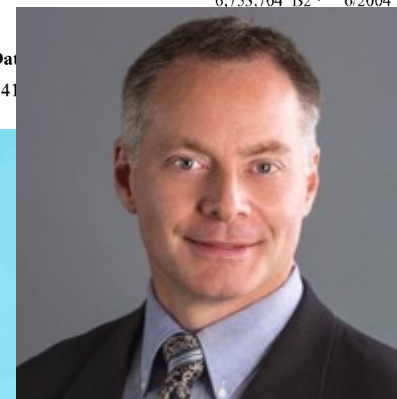


Ron Oliver
Impinj Fellow




Energy Harvesting

Oliver Charge Pump Operation

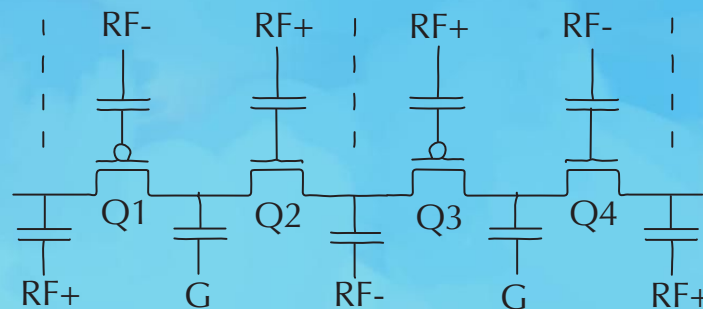

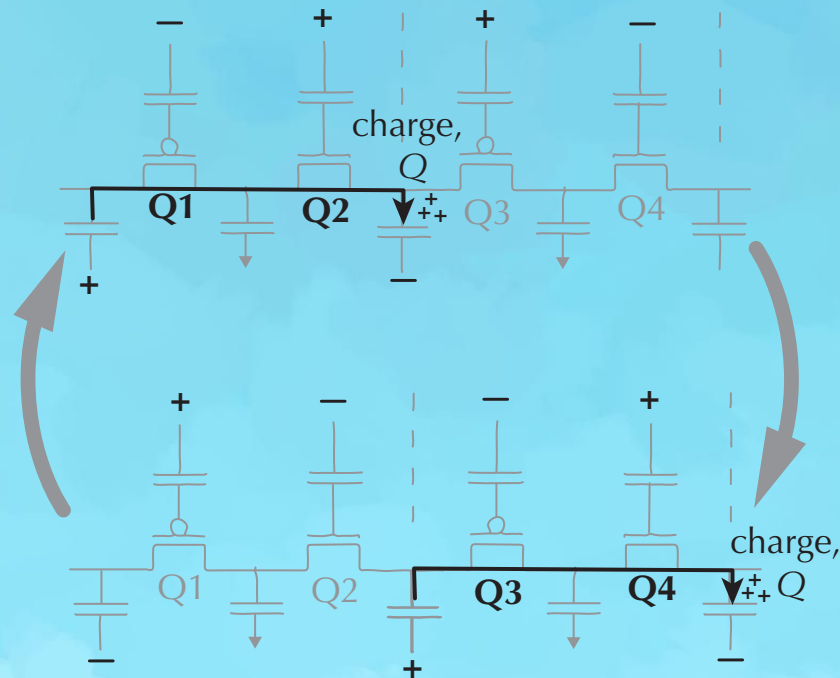
Operation of a Single-Path Rectifier (Two Phases Shown)



RF Input Voltage (positive swing)




RF Input Voltage (negative swing)

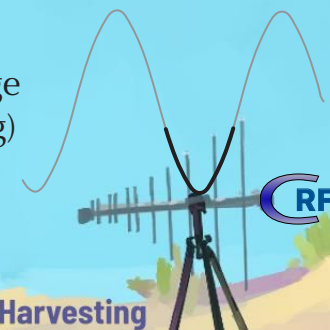

Notes on CMOS Charge Pumps

- Mandal charge pump is simpler to design because it self-biases
- Oliver charge pump is less efficient per stage than Mandal – unless the gates are biased (then it becomes more efficient than Mandal)
- Historical bifurcation in the usage among different RFID types due to these CMOS pumps
 - Inductive RFID – Mandal charge pumps and variations since voltage level is rarely an issue
 - UHF RFID – Oliver charge pumps and variations due to range and voltage requirements

Boosting the Voltage

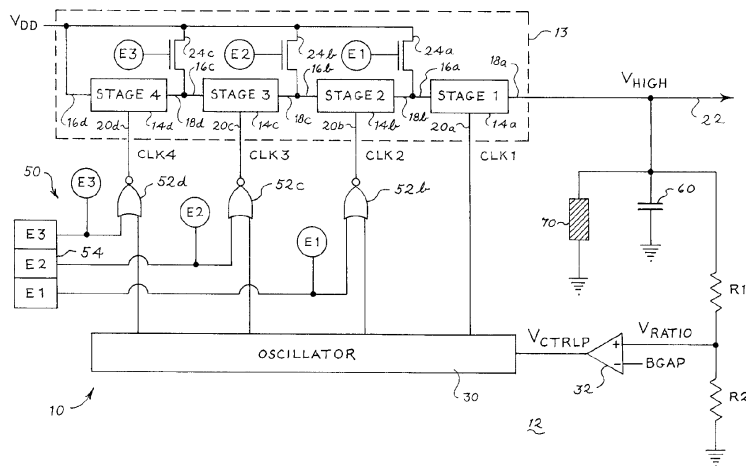

US006486728B2

(12) **United States Patent**
Kleveland

(10) **Patent No.:** **US 6,486,728 B2**
(45) **Date of Patent:** **Nov. 26, 2002**

(54) **MULTI-STAGE CHARGE PUMP**

(75) **Inventor:** **Bendik Kleveland**, Los Altos, CA (US)

(73) **Assignee:** **Matrix Semiconductor, Inc.**, Santa Clara, CA (US)

(*) **Notice:** Subject to any disclaimer, the term of this patent is extended or adjusted under 35 U.S.C. 154(b) by 0 days.

(21) **Appl. No.:** **09/809,878**

(22) **Filed:** **Mar. 16, 2001**

(65) **Prior Publication Data**

US 2002/0130701 A1 Sep. 19, 2002

(51) **Int. Cl.**⁷ **G05F 3/02**

(52) **U.S. Cl.** **327/536; 327/390; 327/539**

(58) **Field of Search** **327/536, 534, 327/390, 539, 598, 590; 323/312, 313, 314**

5,680,300 A	10/1997	Szepesi et al.	363/59
5,781,473 A	7/1998	Javanifard et al.	365/185.18
5,801,987 A	9/1998	Dinh	365/185.18
5,912,552 A	6/1999	Tateishi	323/258
5,994,885 A	11/1999	Wilcox et al.	323/258
6,157,242 A	* 12/2000	Fukui	327/536

* cit

Prin
Assi

(74)
Lior


(57)

An i
mult

of t
voltage

pump

man
of the

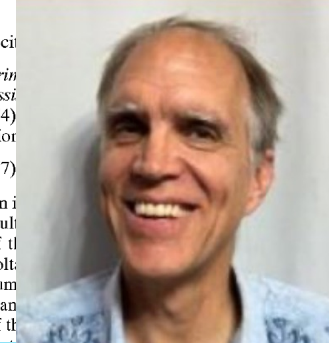

Gilson &

ump having
A first one
to the high
ning charge
p stage in a
mped by all
pped by the

Bendik Kleveland
Matrix/Entrepreneur




Energy Harvesting


**IEEE
RFID
2026**

Greg Durgin


DC-to-DC Conversion

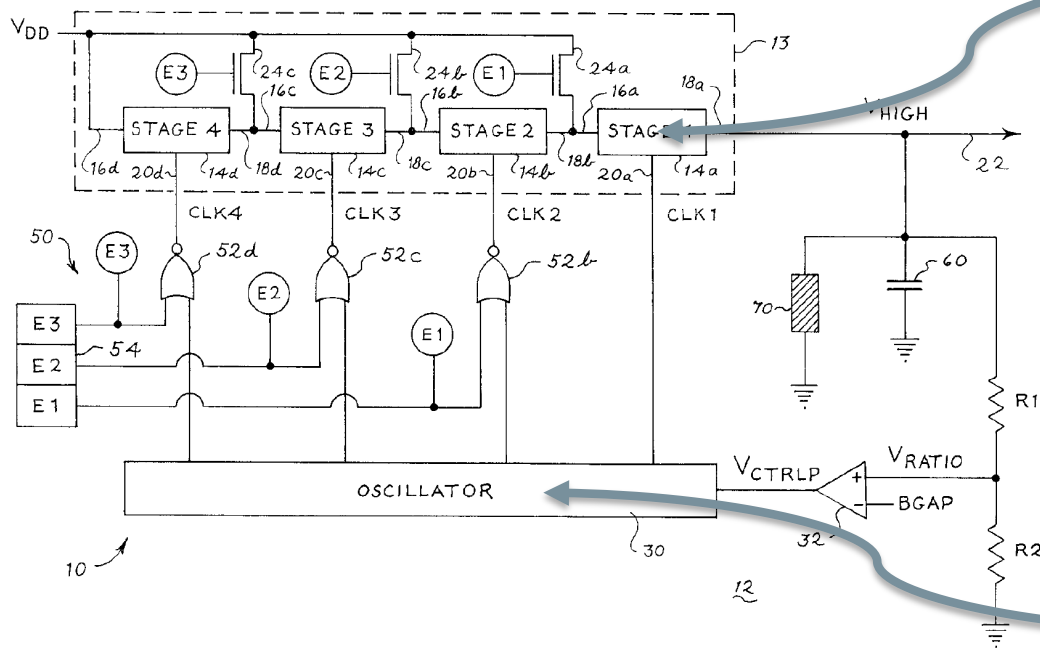

"Throttleable" Charge Pump

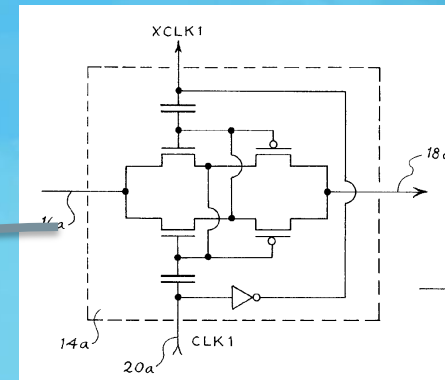

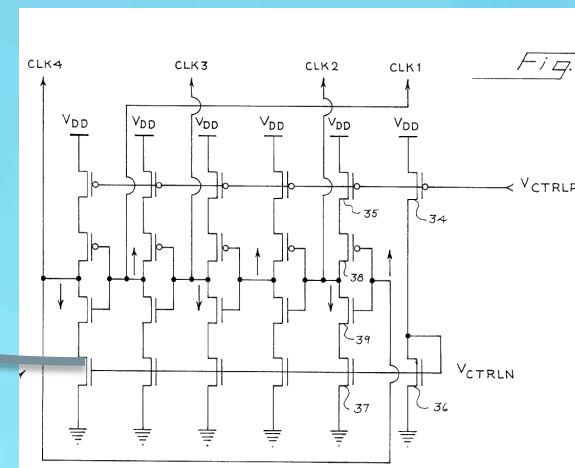Mandal-like rectifier driven by digital clock instead of RF



Ring Oscillator with control line

The Future


IEEE
RFID
2026

Greg Durgin


Energy Harvesting




Exotic Devices

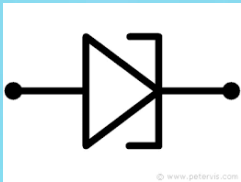


Tunnel diodes

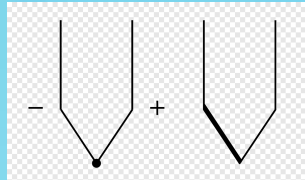


Thermoelectric conversion

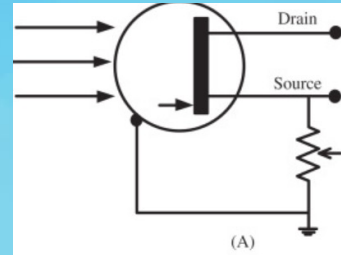


Pyroelectric conversion

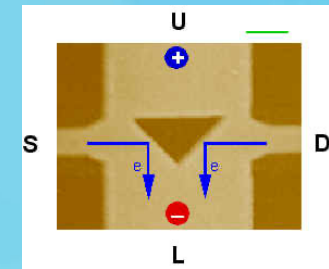

Ballistic Diodes

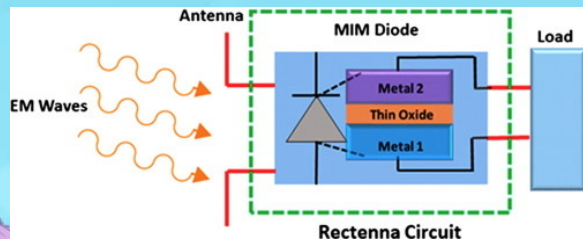

MIM Diodes

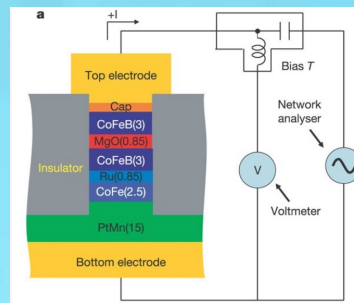

Spin Diodes



A Bright Idea?



Energy Harvesting

The Ending

IEEE
RFID
2026

Greg Durgin

Energy Harvesting

